

## 8.6 The Unit Step Source

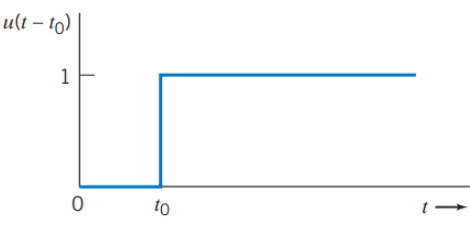


FIGURE 8.6-1 Unit step forcing function,  $u(t - t_0)$ .

$$u(t - t_0) = \begin{cases} 0 & t < t_0 \\ 1 & t > t_0 \end{cases} \quad (8.6-1)$$

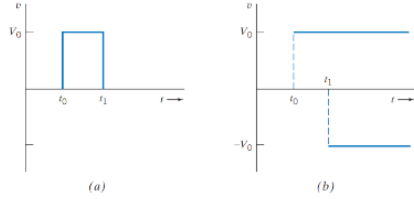


FIGURE 8.6-3 (a) Rectangular voltage pulse. (b) Two-step voltage waveforms that yield the voltage pulse.

Let us consider the pulse source

$$v(t) = \begin{cases} 0 & t < t_0 \\ V_0 & t_0 < t < t_1 \\ 0 & t_1 < t \end{cases}$$

$V_0 u(t)$

A pulse signal has a constant nonzero value for a time duration of  $\Delta t = t_1 - t_0$ .

**P 8.6-3** The input to the circuit shown in Figure P 8.6-3 is the voltage of the voltage source,  $v_s(t)$ . The output is the current in the inductor,  $i_o(t)$ . Determine the output of this circuit when the input is  $v_s(t) = -7 + 13 u(t)$  V.

Sol:

1)


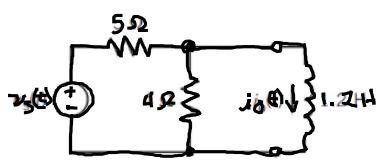
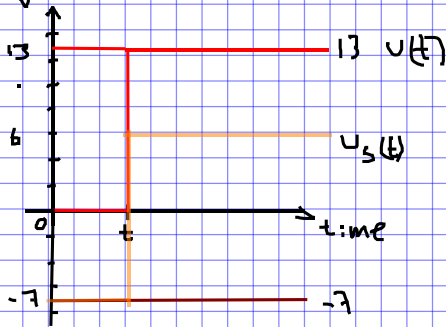


Figure P 8.6-3

$$i_o(t) = ?$$

$$v_s(t) = -7 + 13 u(t) \text{ V}$$


2)

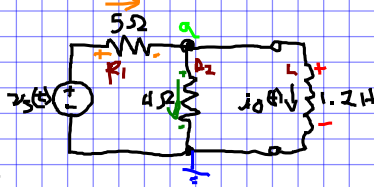


3) Req

$$3.17 \Omega$$

$$R_t = 6V = ?$$

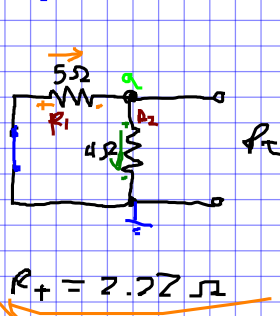

$$R_t = 2.22 \Omega$$

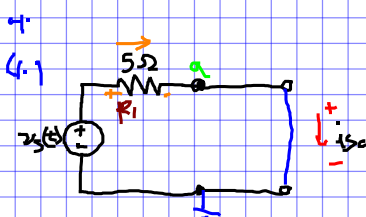

$$i_{sc} = \frac{V_{E_L}}{R_t} = \frac{-7}{5\Omega} = -1.4 \text{ A}$$

t:me < t

$$i(t) = i_{sc} + [i(0) - i_{sc}] e^{-t/\tau} \text{ A}$$

$$i(0) = i_{sc} = -1.4 \text{ A}$$

$$\tau = \frac{L}{R_t} = \frac{1.2 \text{ H}}{2.22 \Omega} = 0.54 \text{ s}$$

$$1/\tau = \frac{R_t}{L} = \frac{2.22 \Omega}{1.2 \text{ H}} = 1.83$$

$$i(t) = -1.4 + [0 - (-1.4)] e^{-1.83t} \text{ A}$$

$$i(t) = -1.4 \text{ A}$$

42)

t:me > t

$$i(t) = i_{sc} + [i(0) - i_{sc}] e^{-t/\tau} \text{ A}$$

$$i(0) = -1.4 \text{ A}$$

$$i_{sc} =$$



$$i_{sc} = \frac{V_{E_L}}{R_t} = \frac{-7 + 13}{5\Omega} = \frac{6 \text{ V}}{5\Omega} = 1.2 \text{ A}$$

$$1/\tau = \frac{R_t}{L} = \frac{2.22 \Omega}{1.2 \text{ H}} = 1.83$$

$$i(t) = 1.2 + [-1.4 - 1.2] e^{-1.83t} \text{ A}$$



$$i(t) = 1.2 - 0.2 e^{-1.83t} \text{ A}$$
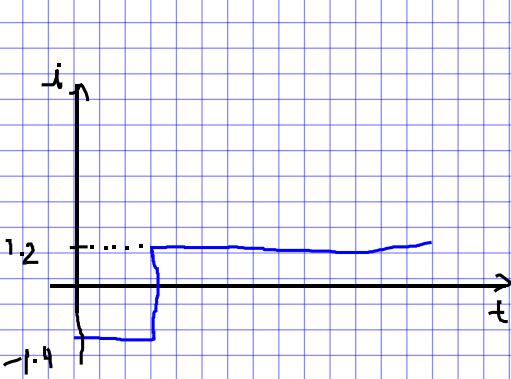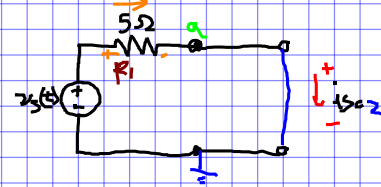
$$i(t) = \begin{cases} -1.4 \text{ A} & t:me < t \\ 1.2 - 0.2 e^{-1.83t} & t:me > t \end{cases}$$



Case 152 16.11.2022

Current Division

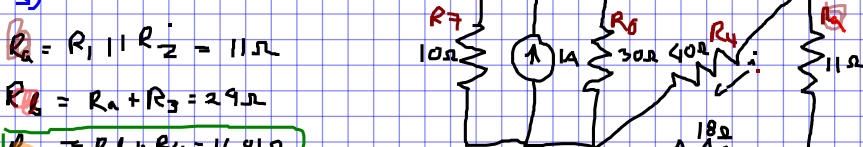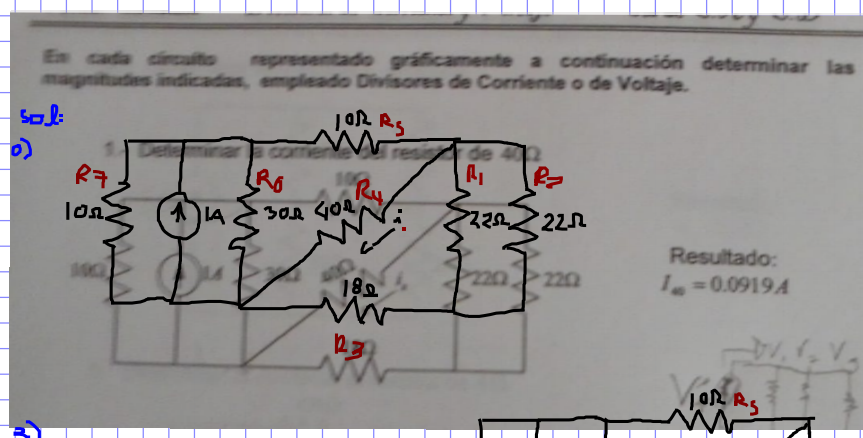

$$R_1 = R_1 \parallel R_2 = 11 \Omega$$

$$R_2 = R_1 + R_3 = 29 \Omega$$

$$R_3 = R_1 \parallel R_4 = 16.81 \Omega$$

$$R_4 = R_3 + R_5 = 26.81 \Omega$$

$$R_5 = R_4 \parallel R_6 = 5.86 \Omega$$

4) Laws,

$$i_{Rx} = \frac{R_p}{R_x} i_p \quad \text{Current Division}$$

Current Division Circuit 6 to 5

$$i_{R4} = \frac{R_T}{R_4} i_T$$

$$= \frac{5.86 \Omega}{26.81 \Omega} 1 \text{ A}$$

$$= 218.57 \text{ mA}$$

Current Division Circuit 4 to 3

$$i_{R4} = \frac{R_5}{R_4} i_{R5}$$

$$= \frac{16.81 \Omega}{40 \Omega} 218.57 \text{ mA}$$

$$i_{R4} = 91.85 \text{ mA}$$

$$i_{R4} = 91.85 \text{ mA}$$

$$i_{R4} = 91.85 \text{ mA}$$

$$i_{R4} = 91.85 \text{ mA}$$

$$i_{R4} = 91.85 \text{ mA}$$