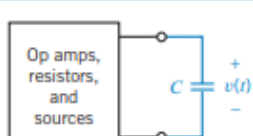


C.6.30 16 10.11.2022


### Section 8.3 The Response of a First-Order Circuit to a Constant Input

Table 8.12-1 Summary of First-Order Circuits
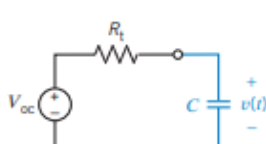
#### FIRST-ORDER CIRCUIT CONTAINING A CAPACITOR



Replace the circuit consisting of op amps, resistors, and sources by its Thévenin equivalent circuit:



The capacitor voltage is


$$v(t) = V_{oc} + (v(0) - V_{oc})e^{-t/\tau}$$

where the time constant  $\tau$  is


$$\tau = R_t C$$

and the initial condition  $v(0)$  is the capacitor voltage at time  $t = 0$ .
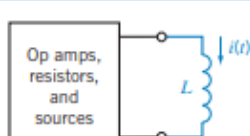
#### FIRST-ORDER CIRCUIT CONTAINING AN INDUCTOR



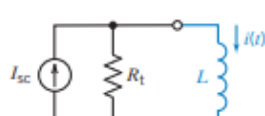Replace the circuit consisting of op amps, resistors, and sources by its Norton equivalent circuit:



The inductor current is


$$i(t) = I_{sc} + (i(0) - I_{sc})e^{-t/\tau}$$

where the time constant  $\tau$  is

$$\tau = \frac{L}{R_t}$$

and the initial condition  $i(0)$  is the inductor current at time  $t = 0$ .

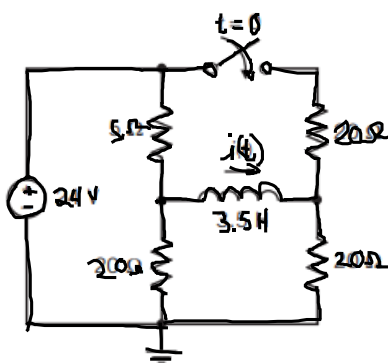**P 8.3-20** The circuit shown in Figure P 8.3-20 is at steady state before the switch closes. Determine  $i(t)$  for  $t \geq 0$ .



1)  $i(t) = ?$

$$= i_{sc} + [i(0) - i_{sc}]e^{-t/\tau}$$

$i_{sc} = ?$


$i(0) = ?$

$\tau = \frac{L}{R_t} = ?$



$R_t = ?$

Figure P 8.3-20




2) Label

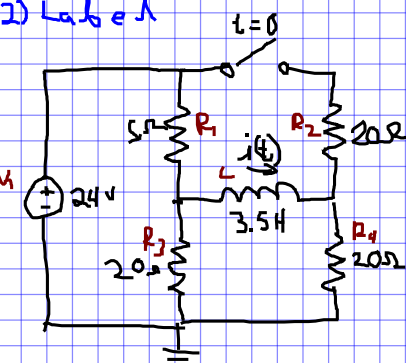


3) 3.1)  $R_t$

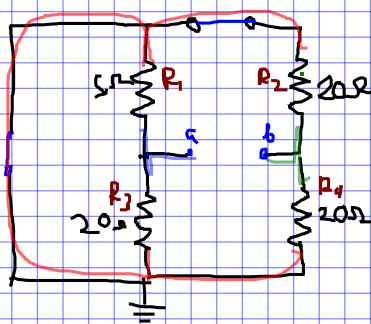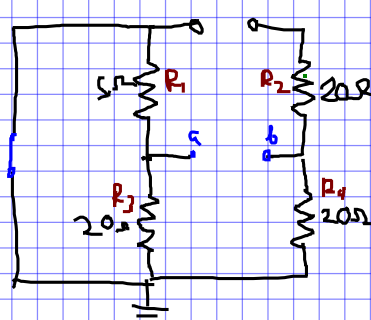

3.2)  $i(0)$

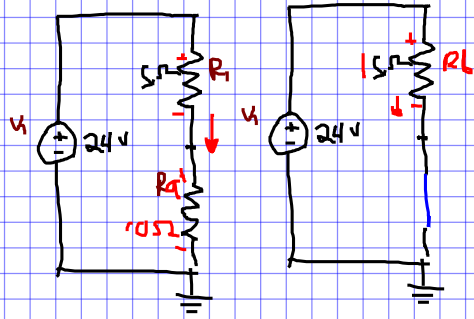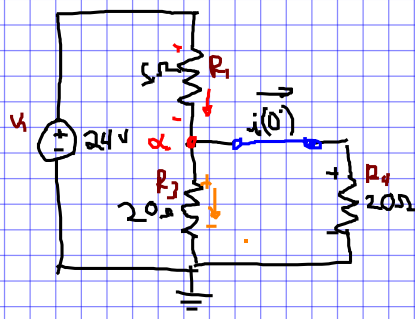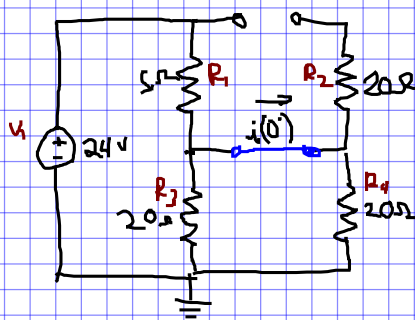

2.3

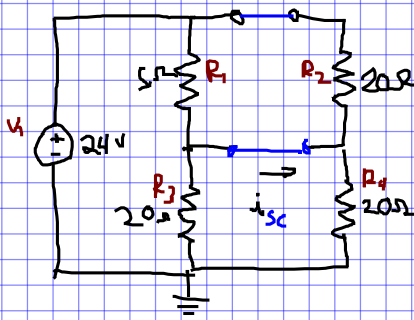

H.A

4.2

$$i_{R_1} = \frac{V_1}{R_1}$$

$$= \frac{24V}{15\Omega}$$

$$= 1.6A$$

$$i(0) = \frac{R_2}{R_4} i_{R_1}$$

$$= \frac{10\Omega}{20\Omega} 1.6A$$

$$= 800mA$$